


problem1 - Seqdet

mealy sequence detector

Goal: pattern 1101, overlap

FSM State Transition Diagram

mealy fsm (arcs indicates input/output)

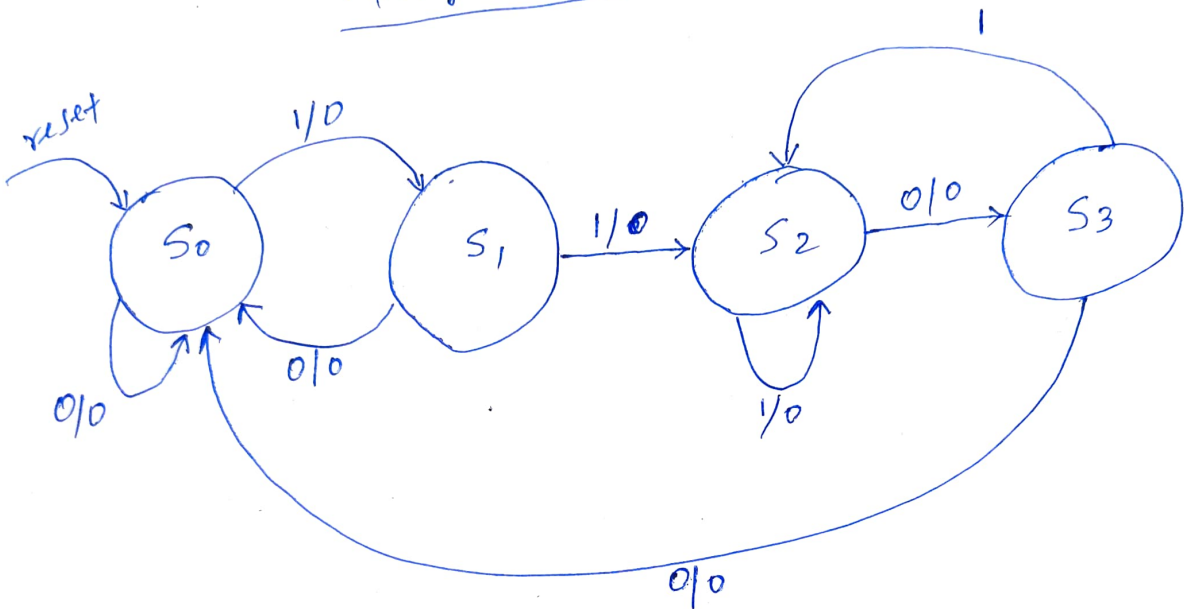

FSM State Transition Table

<u>current state</u>	<u>input</u>	<u>Next state</u>
S0	0	S0
S0	1	S1
S1	0	S0
S1	1	S2
S2	0	S3
S2	1	S2
S3	0	S0
S3	1	S1

State encoding

we have used
binary encoding over
one-hot encoding because
in one-hot encoding
we need one designated
bit for each state.
✓ which requires more flips-flops.

state	Encoding
S_0	00
S_1	01
S_2	10
S_3	11

Current

→ FSM Encoded State Transition Table

Current state		Input X	Next state	
S_1	S_0		S_1'	S_0'
0	0	0	0	1
0	0	1	0	0
0	1	0	1	0
0	1	1	1	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	1
1	1	1	0	1

Next-state & output logic

$$S_1' = (S_1 \cdot \bar{S}_0 + \bar{S}_1 \cdot S_0 \cdot X)$$

$$S_0' = \bar{S}_1 \cdot \bar{S}_0 \cdot X + (S_1 \cdot (\bar{S}_0 \cdot \bar{X} + S_0 \cdot X))$$

$$\text{or } S_0' = \bar{S}_1 \cdot \bar{S}_0 \cdot X + S_1 \cdot X \text{ NOR } X$$

$$Y = S_1 \cdot S_0 \cdot X$$

only high when ~~Current state~~ Current state = $S_3(11)$ & $X=1$.